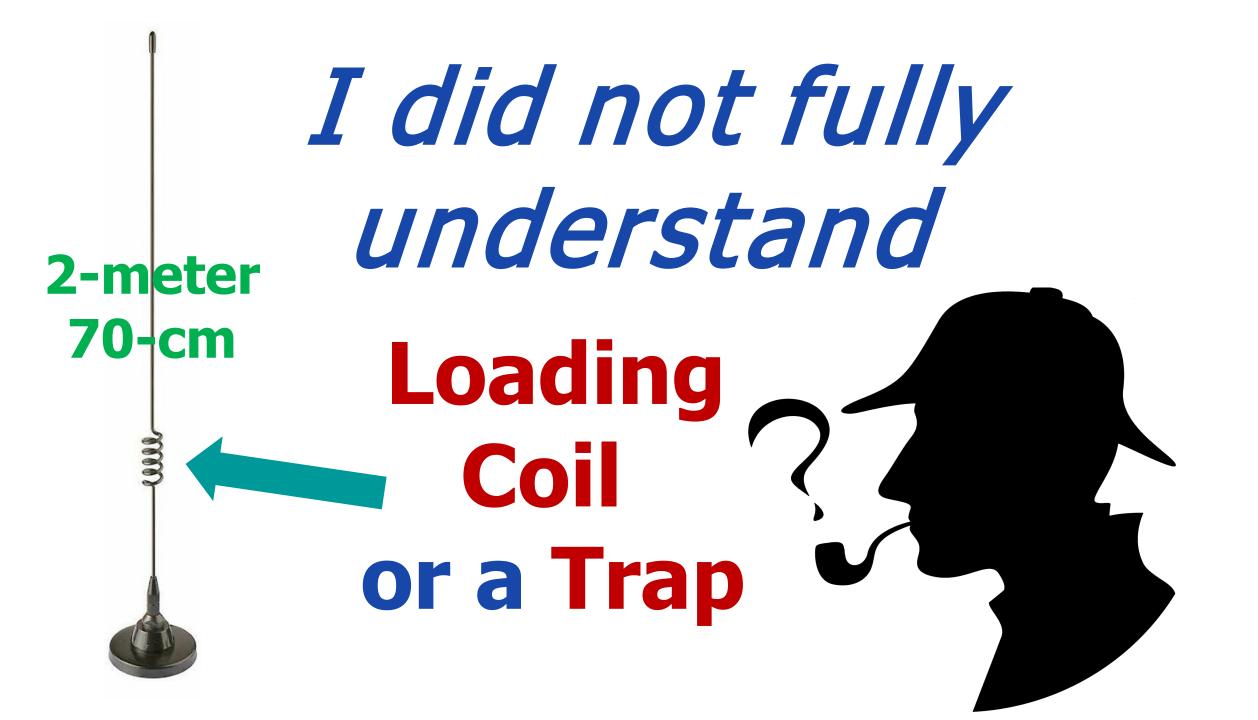
The Difference Between Loading Goils and Traps, Also Self-Resonant Trans



1978: Sean Connery. Donald Sutherland, Lesley-Anne Down

Traps & Loading Coils Differences Similarities Still Undiscovered Country

w6nbc/com/slides



Loading Coils




Just a Plain Coil to add inductance to make a short antenna work on a lower frequency




A Full-size 32 ft. 1/4 wavelength whip



Important Single-Band Device

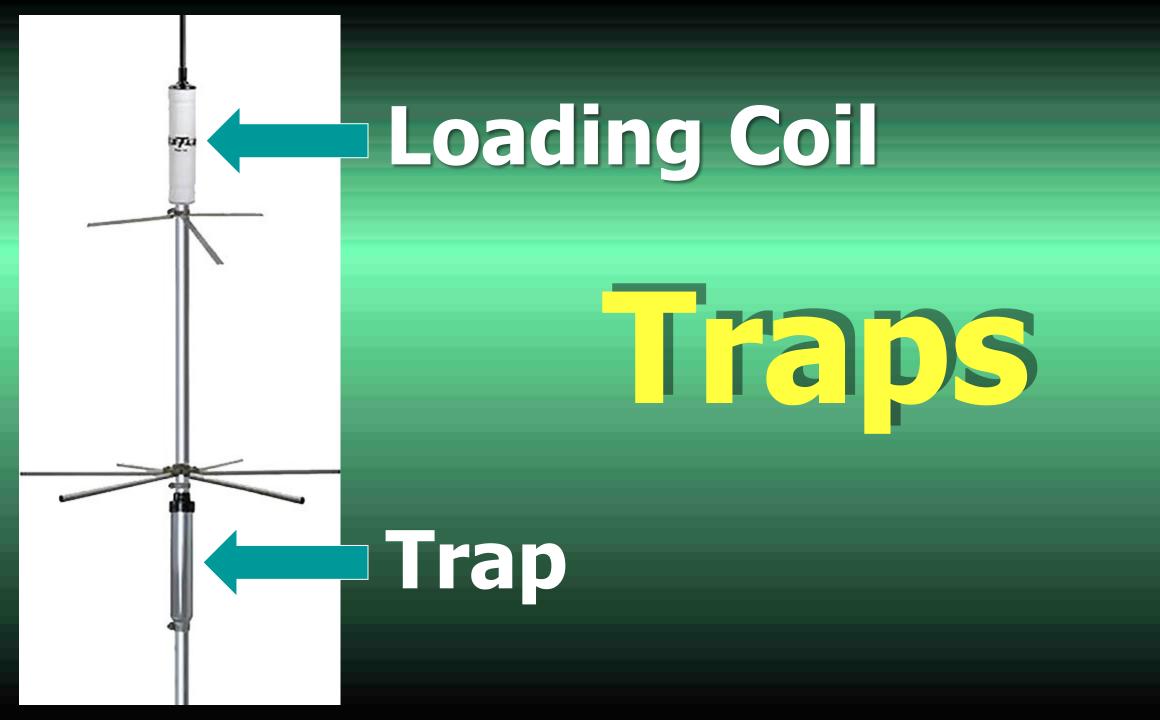


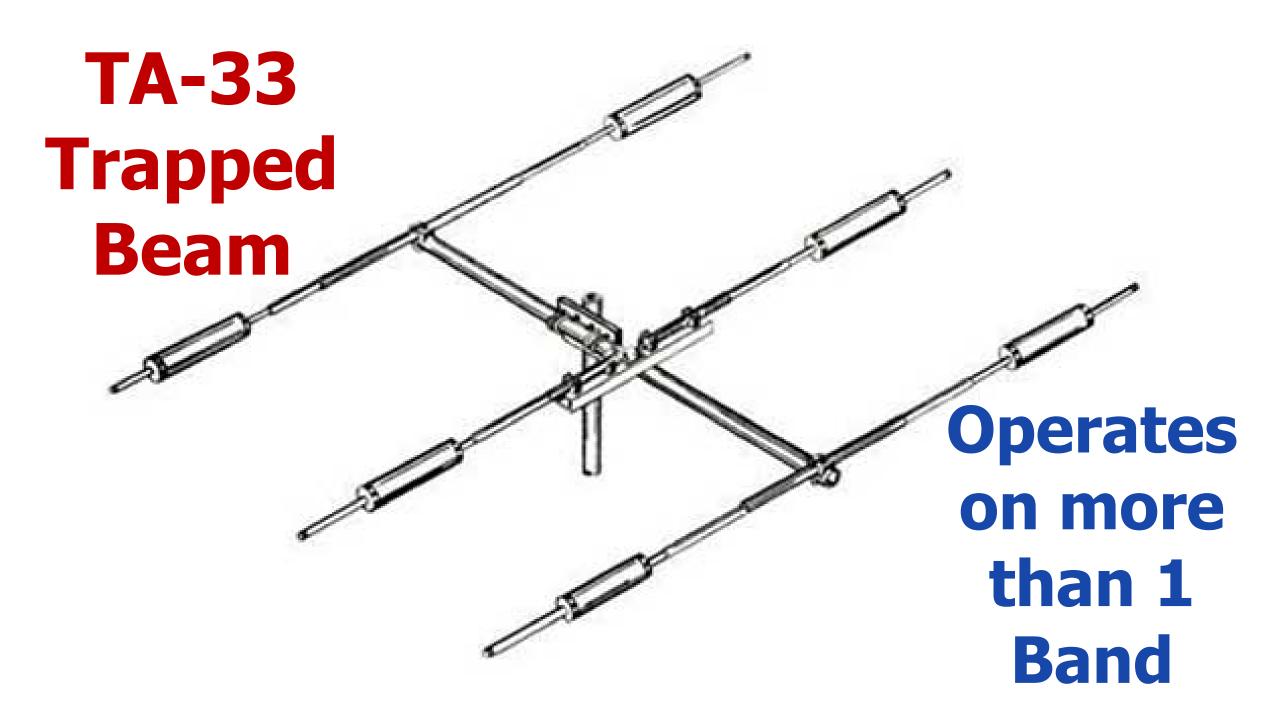

Multi-80m **Band Device 40**m **20**m 15m CHIHININ **10**m


5BTV Hustler **Multi-Band Trapped Vertical**

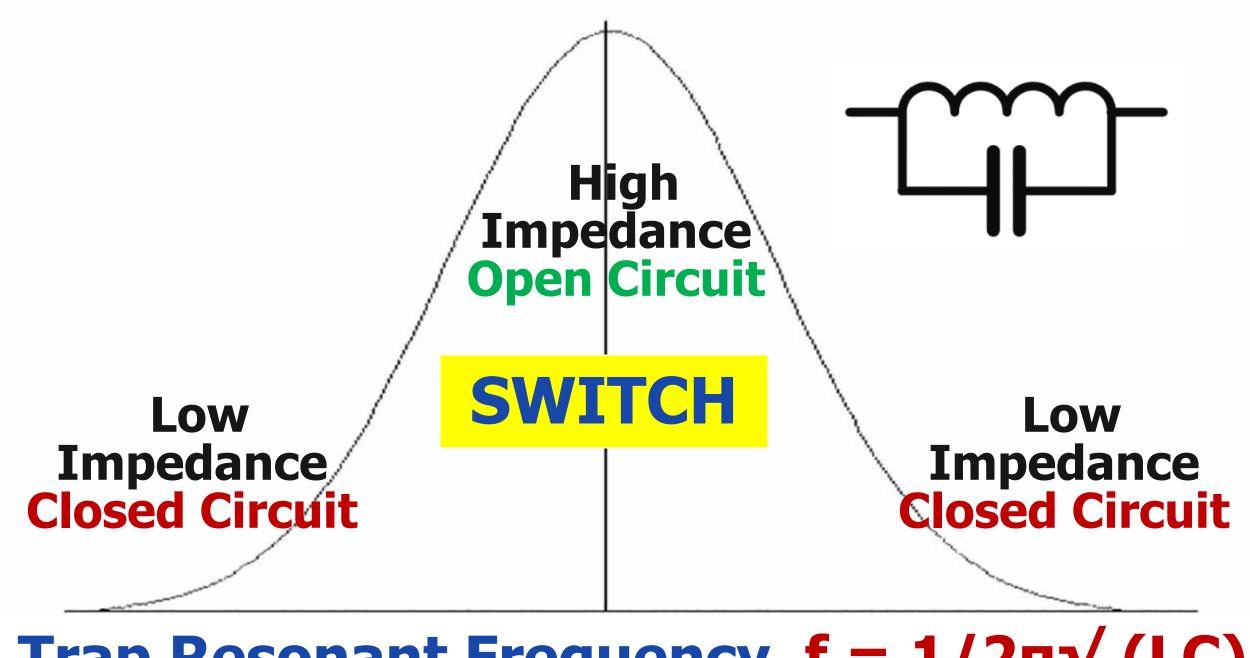Electrically AThapdis a Coil in Parallephathaincaplacitor




Trap Resonant Frequency $f = 1/2\pi\sqrt{(LC)}$

OPEN Only the inner dipole works

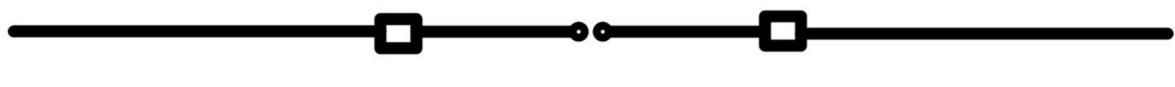


CLOSEDThe whole dipole works

Tri-Band Inverted V

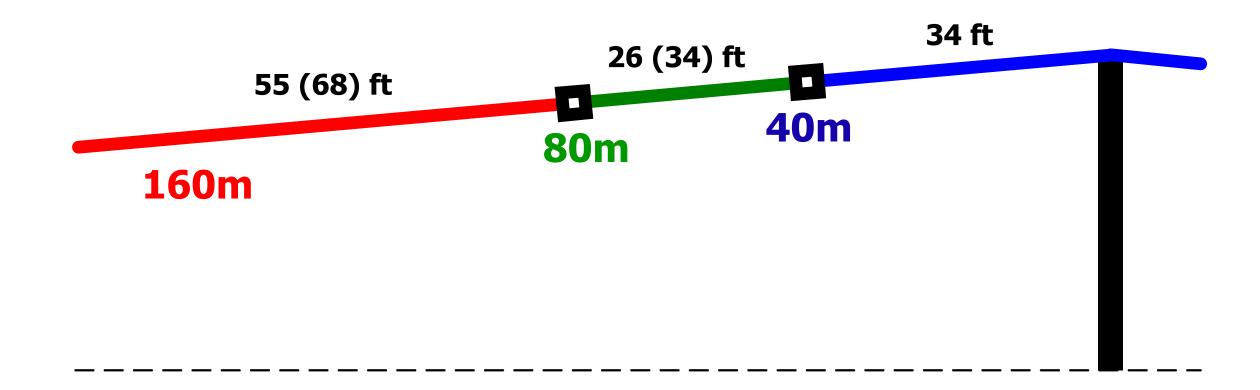



Traps Made of Coax

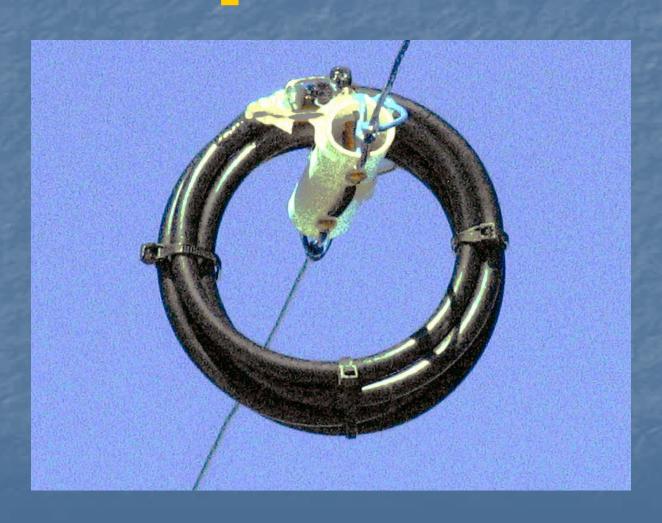



Parallel L & C From Coax

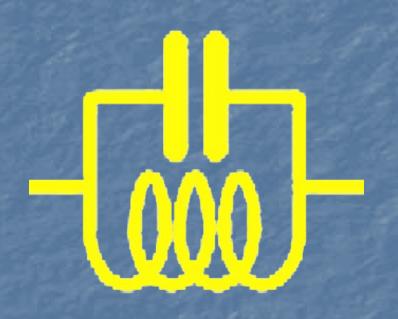

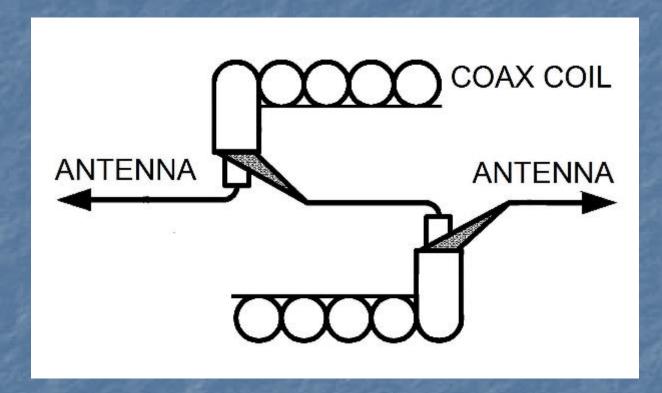


Outside of Coax is L Inside of Coax is C In parallel


Scramble Wound Trap





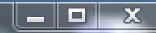

Coaxial Trap Design

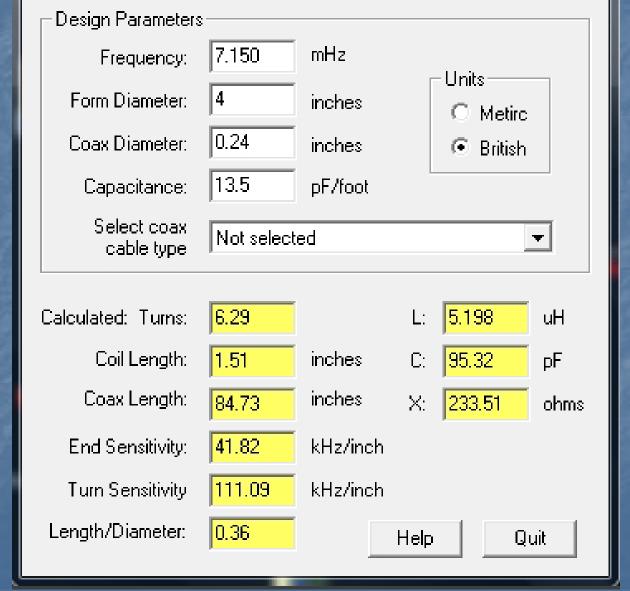


Coaxtrap.zip

Trapqsl.net/ve6yp/





PCB TRAPS: L & C

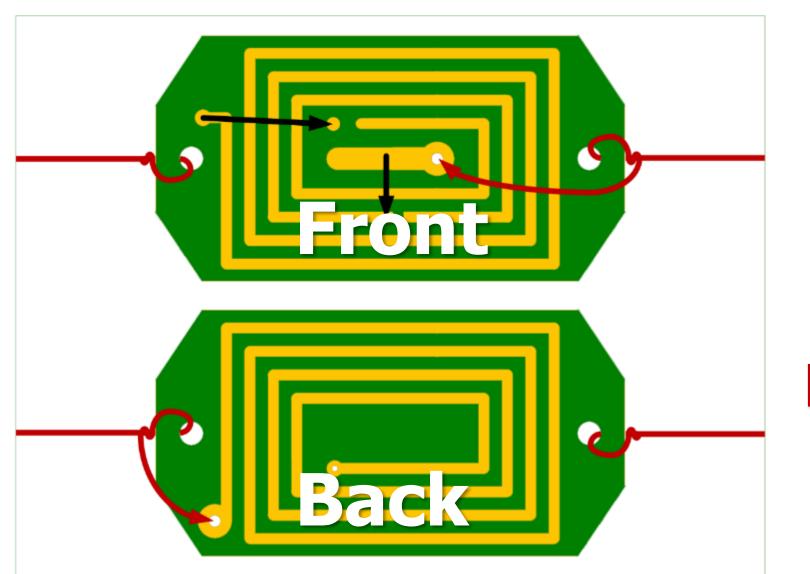



Inductance: PCB Coil(s)

Capitance:
Back-to-Back
PCB Stripline

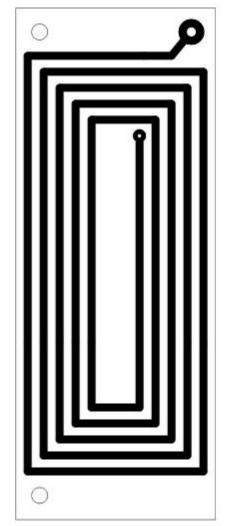

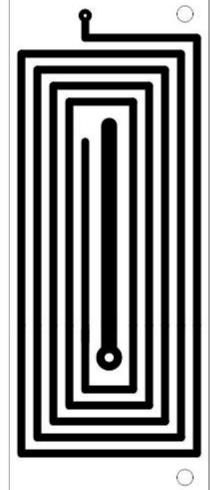

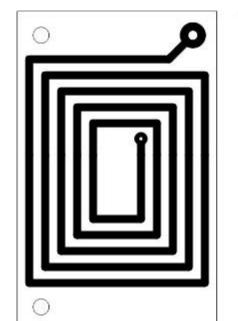

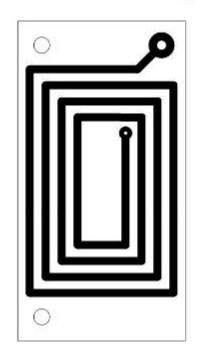




PCB etching patterns


3 boards cover all HF bands down to 40m

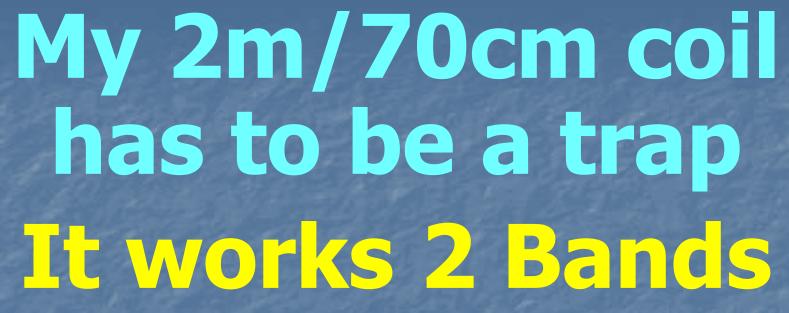I thought that was all all I negled to know about traps But still a Mystery





But where's the capacitor?

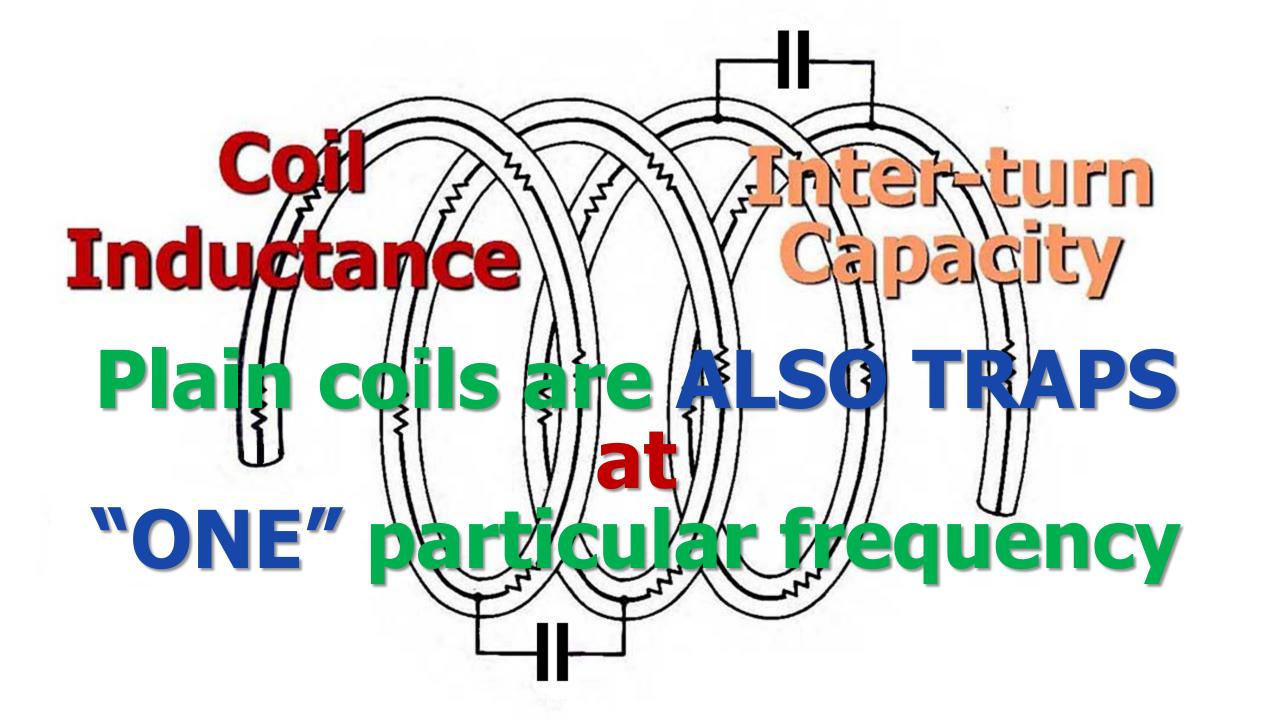

Self-Resonant Frequency

High Impedance Open Circuit

Low Impedance Closed Circuit

No added

Capacitor


Low Impedance Closed Circuit

Frequency

DASIGNINGA 2m-70gm-6m-4 S-R Trapped Dipoe

Pick a Set of Coil Parameters Specifically for S-R

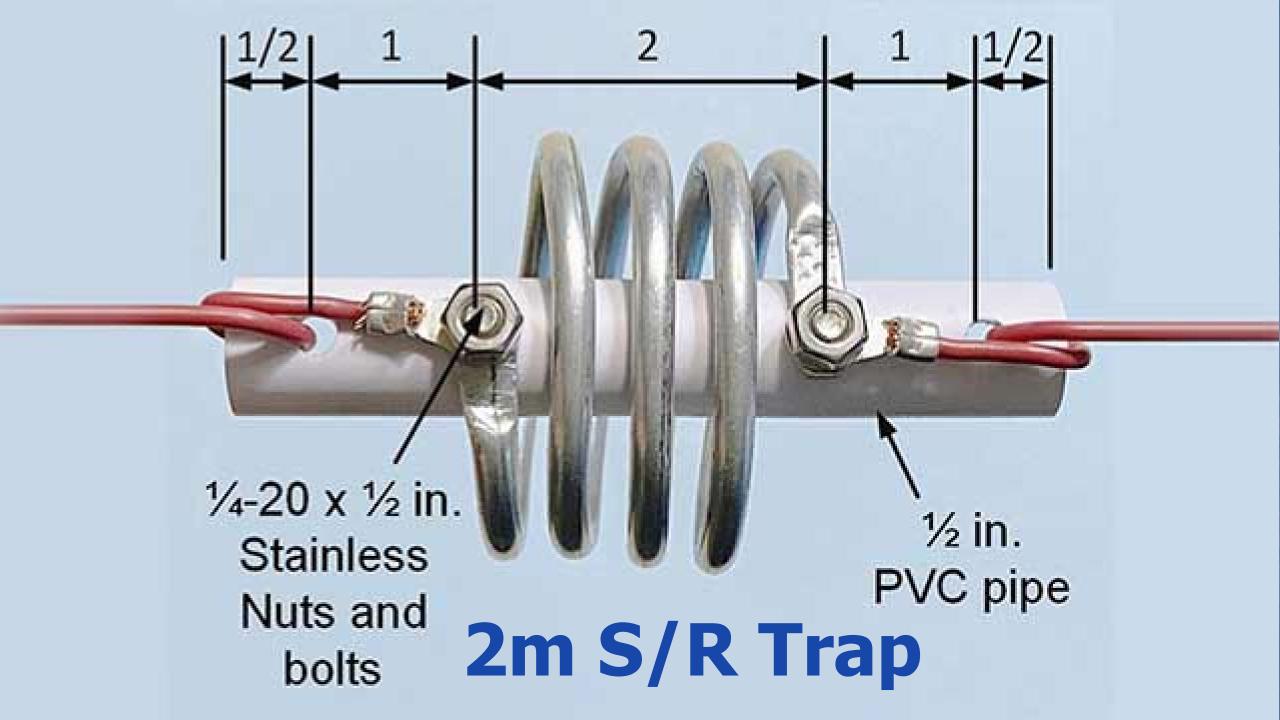- A Diameter
- A Number of Turns
- A Turn Spacing -- Length
- That Creates Self-Resonance



https://www.teslascientific.com/products/coil-resonant-frequency-calculator/


Enter the Coil Length, Coil Diameter, and Number Of Turns		
Coil Length	2	Inches
Coil Diameter	2	Inches
Number Of Turns	4	
Conductor Length	25.133	Inches
Resonant Frequency	140.127	Megacycles/sec ~







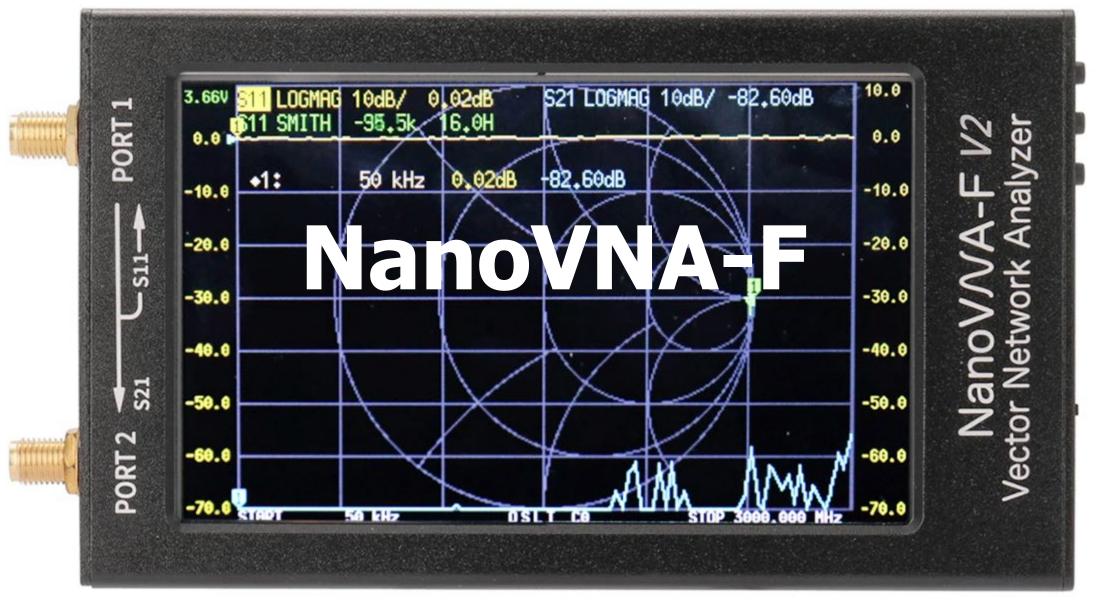
Trap "dips" At the Self-Resonant Frequency





S21 Thru 2-port measurement




With 1 Pair of (70cm) Traps

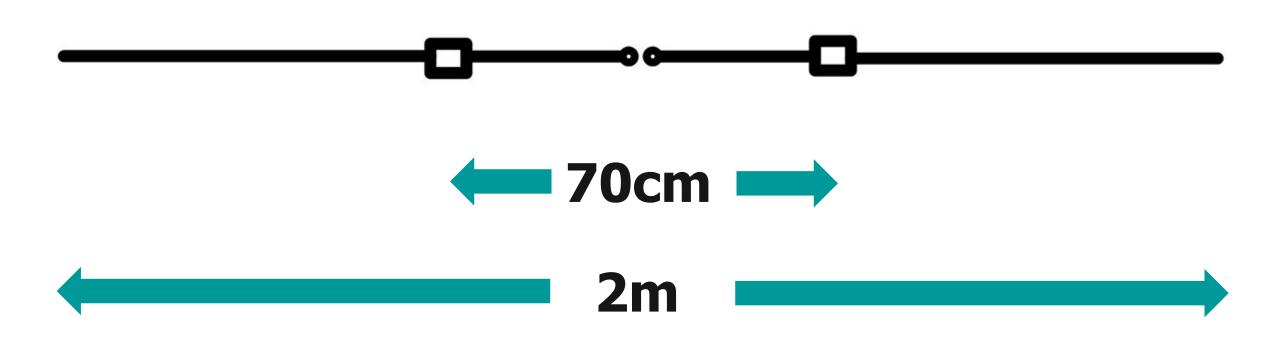


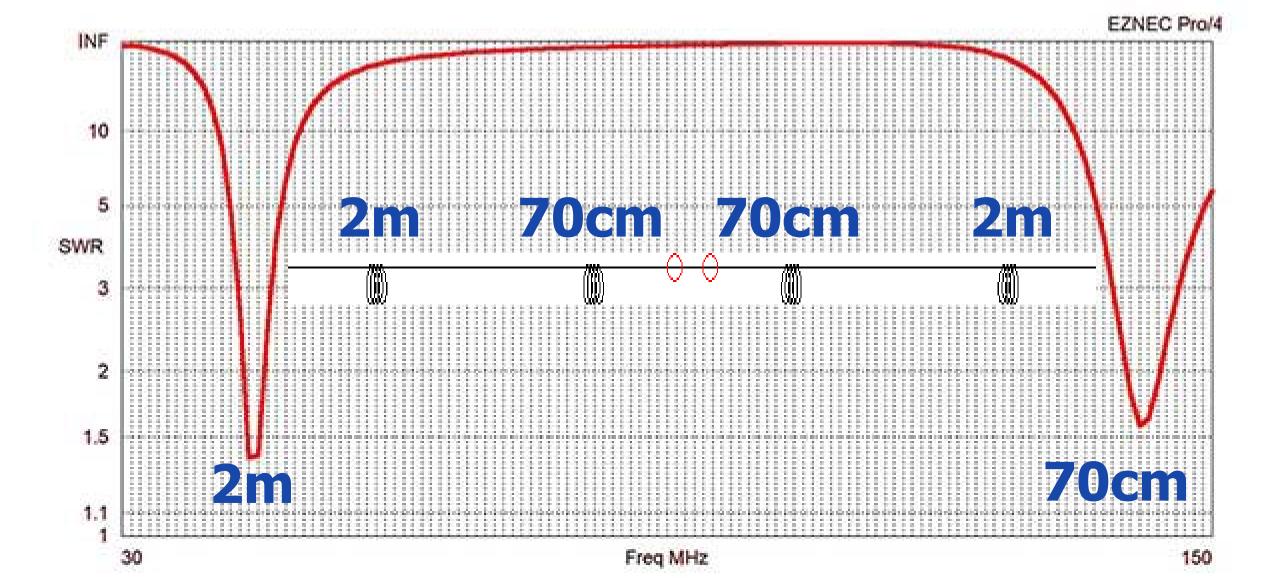

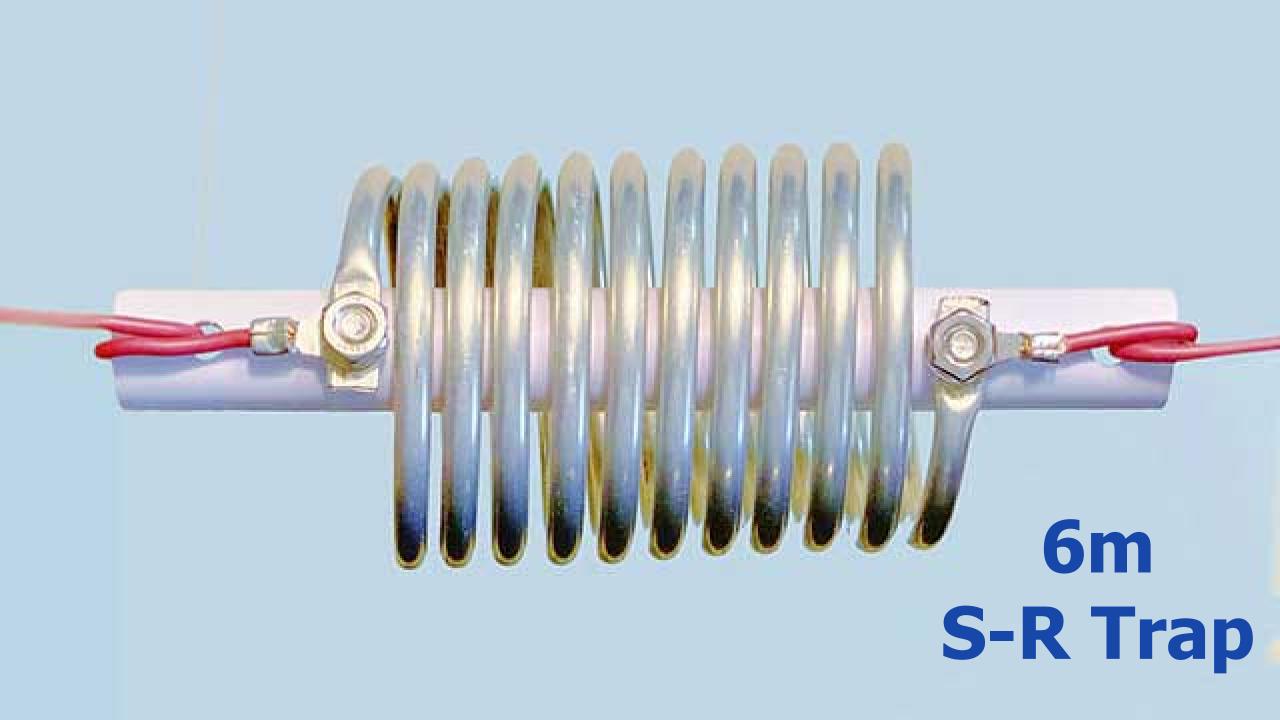

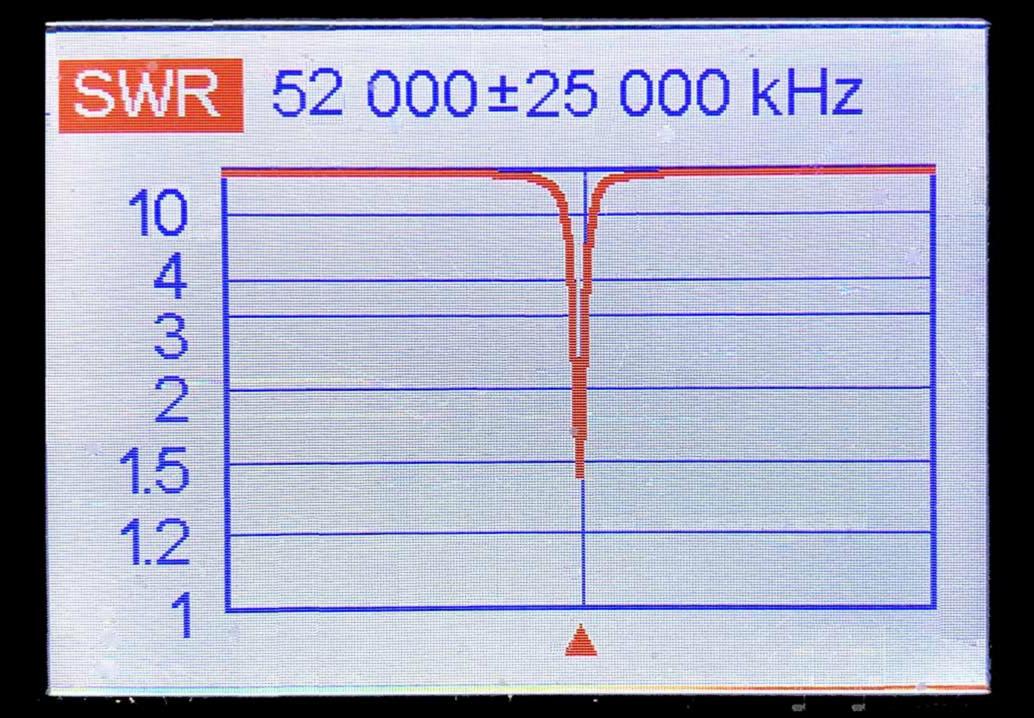


70 Gm, 2m, 6m, 8m Hanne Barrell Research

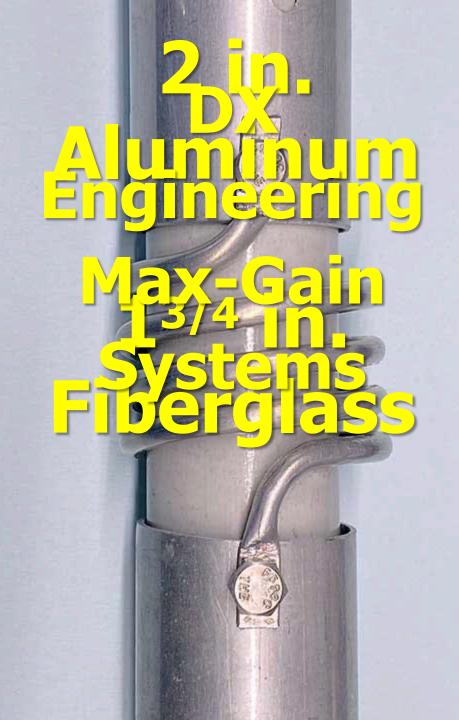

In Development 10m/6m/2m/70cm Coaxially-fed 1/2 Wavelength **No-radial** Free-standing 18 ft. Vertical or Flagpole

In Development

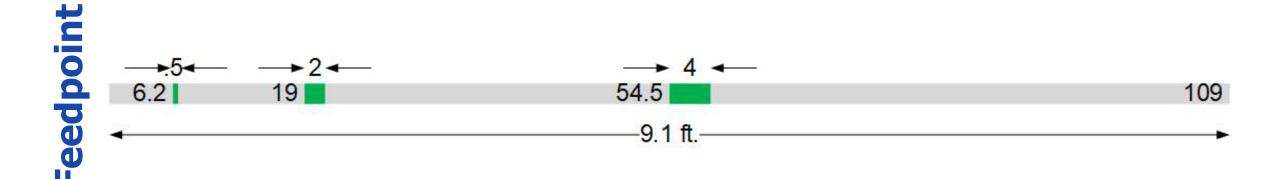1/2 of 18/20 ft. <u>Vertical</u> or Disguised Flagpole




At Lower Frequency

S-R Traps may be too large or heavy

Band	Turns	Coil Length in.
70-cm	1	0.5
220 MHz	2	1
2-meters	4	2
6-meters	1 3	6.5
10-meters	30	15
15-meters	42	21
17-meters	50	25
20-meters	68	34

At Lower Frequency

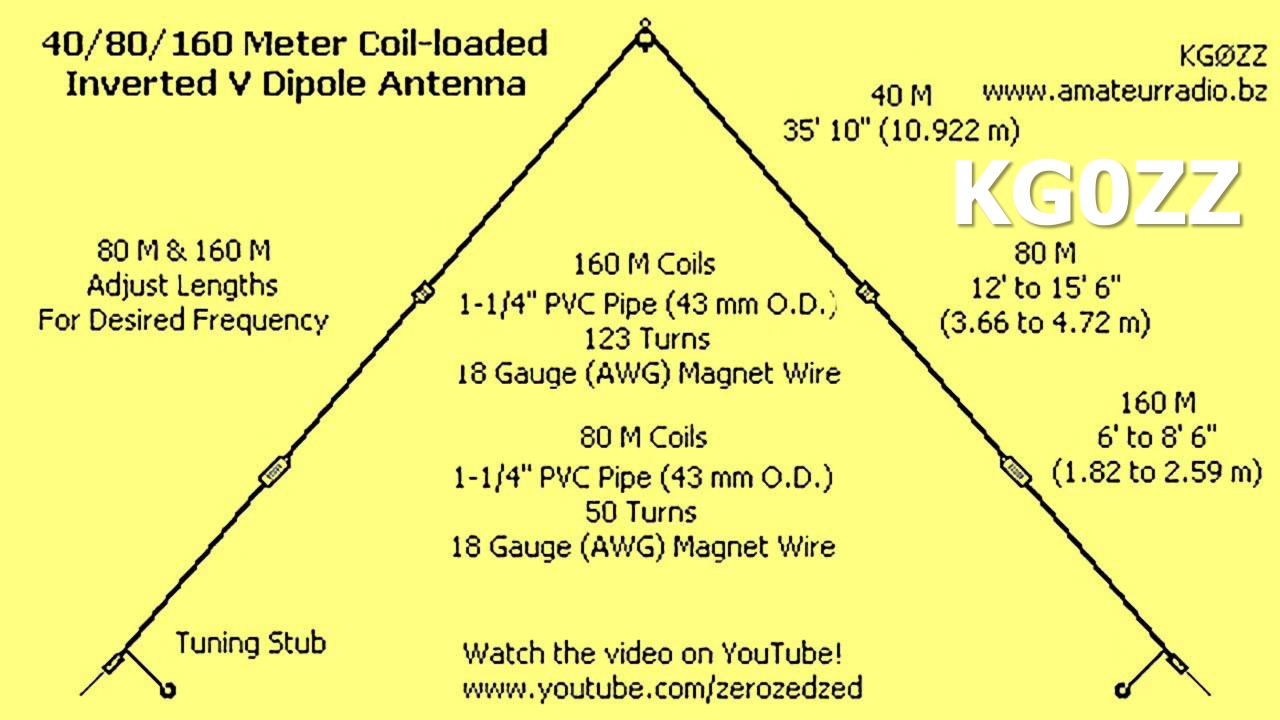- Lower efficiency coils
- Smaller, closer-together windings
- Larger diameter coil







https://www.teslascientific .com/products/coilresonant-frequencycalculator/



So What is it?

2-meter Loading 7 Coil or a Trap





w6nbc.com

w6nbc.com /slides





w6nbcmail @gmail.com